

## **Part 3**

# **Advanced Arithmetic Hardware**

- Adder
- Multiplier

1

## **Adder**

2

## Rounding Adder, Half Adder

Consider rounding a binary number consisting of integer part and fractional part into an integer.


$$\begin{array}{r} 101111111 \cdot 10101 \\ + 000000001 \\ \hline \text{XXXXXXXXX} \end{array}$$

This rounding process requires an adder with as many bits as there are bits in the integer part. This is because all the integer bits may be "1".

The adder used for rounding purpose need not be constructed from full adders since the basic adder block only need to add two bits together.

3

## Rounding adder

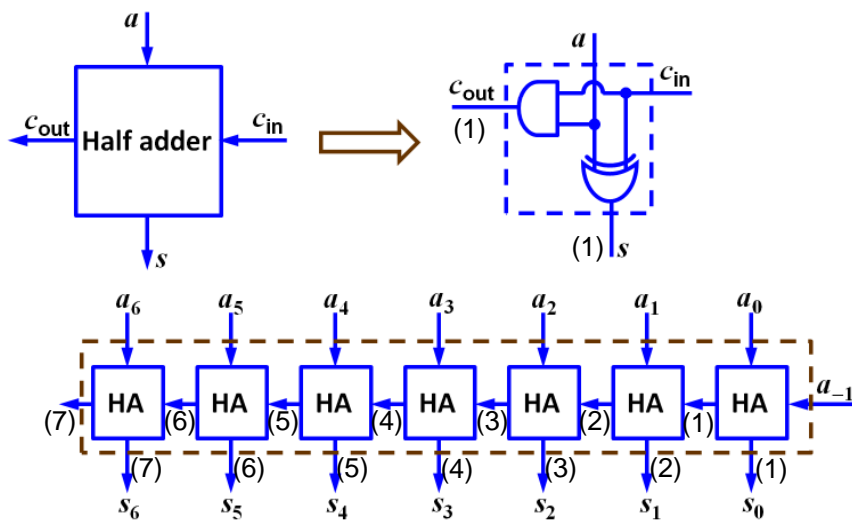


Each half adder needs 1 gate delay. The  $N$ -bit rounding adder needs  $N$  gate delays to complete. This is because the carry bit propagates from stage to stage.

4
 
## Carry Look-Ahead in Rounding Adder

In carry look-ahead, the carry bit does not propagate from stage to stage but is computed separately.



Example: This carry is a "1" provided that  $a_4$ ,  $a_3$ ,  $a_2$ ,  $a_1$ ,  $a_0$ , and  $a_{-1}$  are "1".

Thus, carry =  $(a_4 \bullet a_3 \bullet a_2 \bullet a_1 \bullet a_0) \bullet a_{-1}$ .

$(a_4 \bullet a_3 \bullet a_2 \bullet a_1 \bullet a_0)$  can be computed separately.


5

Let  $p = a_3 \bullet a_2 \bullet a_1 \bullet a_0$ .

$p$  is computed independent of  $c_{in}$ .

$$c_{out} = p \bullet c_{in}$$

 
If each half adder, or each gate, requires 1 gate delay, then this block consisting of 4 (actually  $3\frac{1}{2}$ ) half adders requires 4 gate delays. However,  $p$  requires only 1 gate delay.



6

Therefore, cascading of such blocks is possible.

 
Carry-out takes 1 (to compute first  $p$ ) + 3 (propagation through 3 gates) = 4 gate delays.



7
 
## Full Adder

Bitwise addition of two 2's complement numbers requires adding not only two input bits but also the carry bit.




$$s_n = a_n \oplus b_n \oplus c_{n-1}$$

$$c_n = a_n \cdot b_n + b_n \cdot c_{n-1} + a_n \cdot c_{n-1}$$


8

# Ripple Carry Adder

 

$c_3$  can be computed only after  $c_2$  has been computed.  
 $c_2$  can be computed only after  $c_1$  has been computed.  
 $c_1$  can be computed only after  $c_0$  has been computed.

9

 


Computing each carry from valid inputs needs 2 gate delays. Therefore, computing  $c_3$  needs 8 gate delays.

In general, an  $N$  stage ripple carry adder needs  $2N$  gate delays to compute  $c_{N-1}$ .

10

## Carry Look-Ahead Adder

 


If  $a_n = b_n = 1$ , the full adder generates a carry, i.e.  $c_n = 1$  regardless of  $c_{n-1}$ .

Let  $g_n$  denotes the state when the  $n^{\text{th}}$  full adder generates a carry. Hence,

$$g_n = a_n \bullet b_n \quad (a_n \text{ AND } b_n)$$

11

 


If, either  $a_n$  OR  $b_n$  is a 1,  $c_n = 1$  if  $c_{n-1} = 1$  and  $c_n = 0$  if  $c_{n-1} = 0$ , i.e. the full adder propagates carry-in to carry-out.

Let  $p_n$  denotes the state when the  $n^{\text{th}}$  full adder propagates a carry. Hence,

$$p_n = a_n \oplus b_n \quad (a_n \text{ XOR } b_n)$$

12


Instead of building this, we build this

 

Carry generation for 1 bit:


$$c_n = g_n + p_n \cdot c_{n-1}$$

 $c_n$  needs 1 gate delay  
to compute  $g_n$  and  $p_n$ ,  
plus 2 gate delays  
= 3 gate delays.



13

Carry generation for 2 bits:

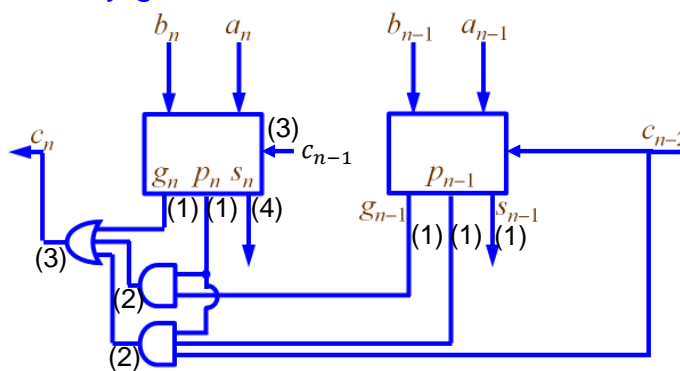

$$c_n = g_n + p_n \cdot c_{n-1}$$

$$c_{n-1} = g_{n-1} + p_{n-1} \cdot c_{n-2}$$


$$c_n = g_n + p_n \cdot \{g_{n-1} + p_{n-1} \cdot c_{n-2}\}$$

$$= g_n + p_n \cdot g_{n-1} + p_n \cdot p_{n-1} \cdot c_{n-2}$$

$c_n$  still takes  
3 gate delays.

14

### Carry generation for 3 bits:

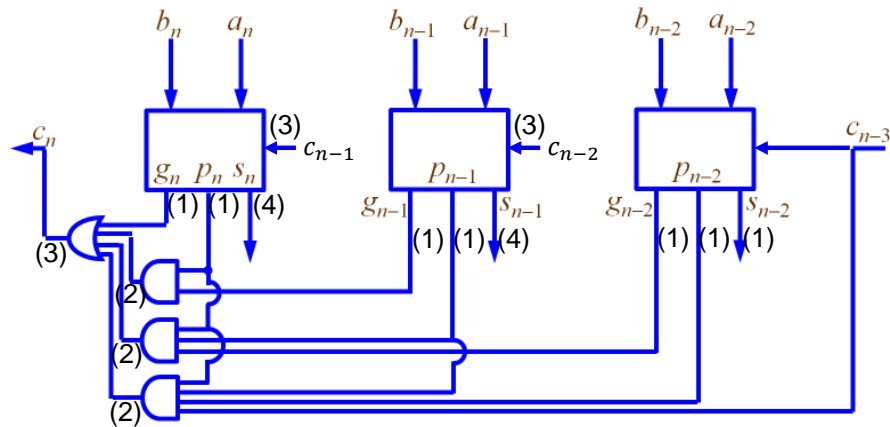

$$c_n = g_n + p_n \bullet g_{n-1} + p_n \bullet p_{n-1} \bullet g_{n-2} + p_n \bullet p_{n-1} \bullet p_{n-2} \bullet c_{n-3}$$

$c_n$  still takes 3 gate delays.

Note that the gate delays will remain 3, 1, 1, 4 for  $c_n$ ,  $g_n$ ,  $p_n$ , and  $s_n$  for any number of bits  $n$ .

15

### Carry generation in general:


$$c_0 = g_0 + p_0 c_{in} = g_0 \text{ OR } (p_0 \text{ AND } c_{in})$$

$$c_1 = g_1 + p_1 c_0 = g_1 + p_1 g_0 + p_1 p_0 c_{in}$$

$$c_2 = g_2 + p_2 c_1 = g_2 + p_2 (g_1 + p_1 (g_0 + p_0 c_{in}))$$

$$c_3 = g_3 + p_3 g_2 + p_3 p_2 g_1 + p_3 p_2 p_1 g_0 + p_3 p_2 p_1 p_0 c_{in}$$

 
$$c_n = g_n + p_n g_{n-1} + p_n p_{n-1} g_{n-2} + \dots + p_n p_{n-1} \dots p_0 c_{in}$$



16



Block state generation:


 


Block generate:  $g_b = g_3 + p_3g_2 + p_3p_2g_1 + p_3p_2p_1g_0$

Block propagate:  $p_b = p_3p_2p_1p_0$

17

  Carry generation for block carry look-ahead adder is the same as the bit-wise carry look-ahead adder.




Note that the gate delays will remain 3, 2, 11, 9, 7, 5 for  $g_b$ ,  $p_b$ ,  $s_{n-1}$  to  $s_{n-4}$  for any number of blocks.

18

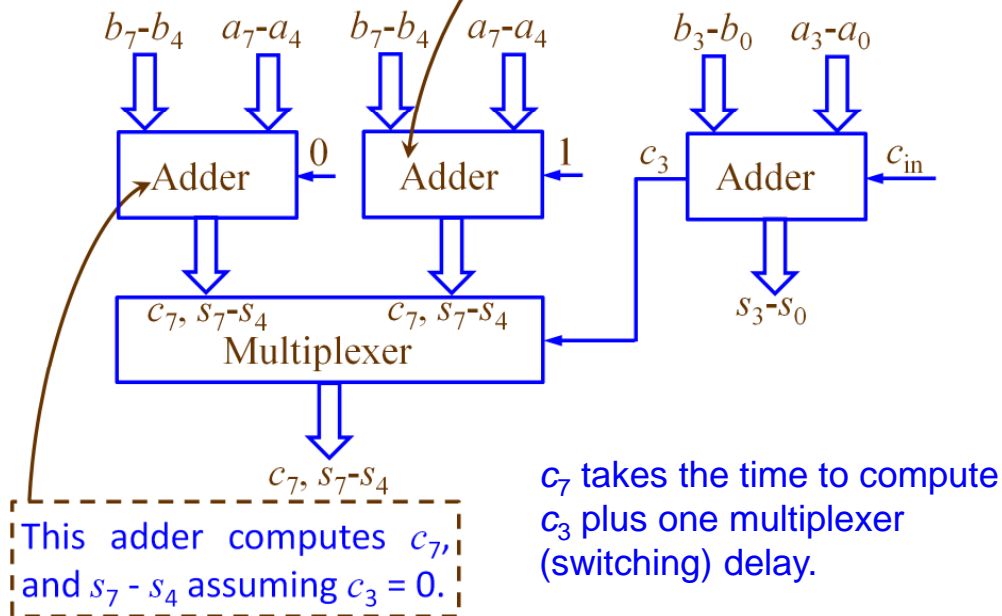
## Carry Select Adder

This adder computes  $c_7$  and  $s_7 - s_4$  assuming  $c_3 = 1$ .



19

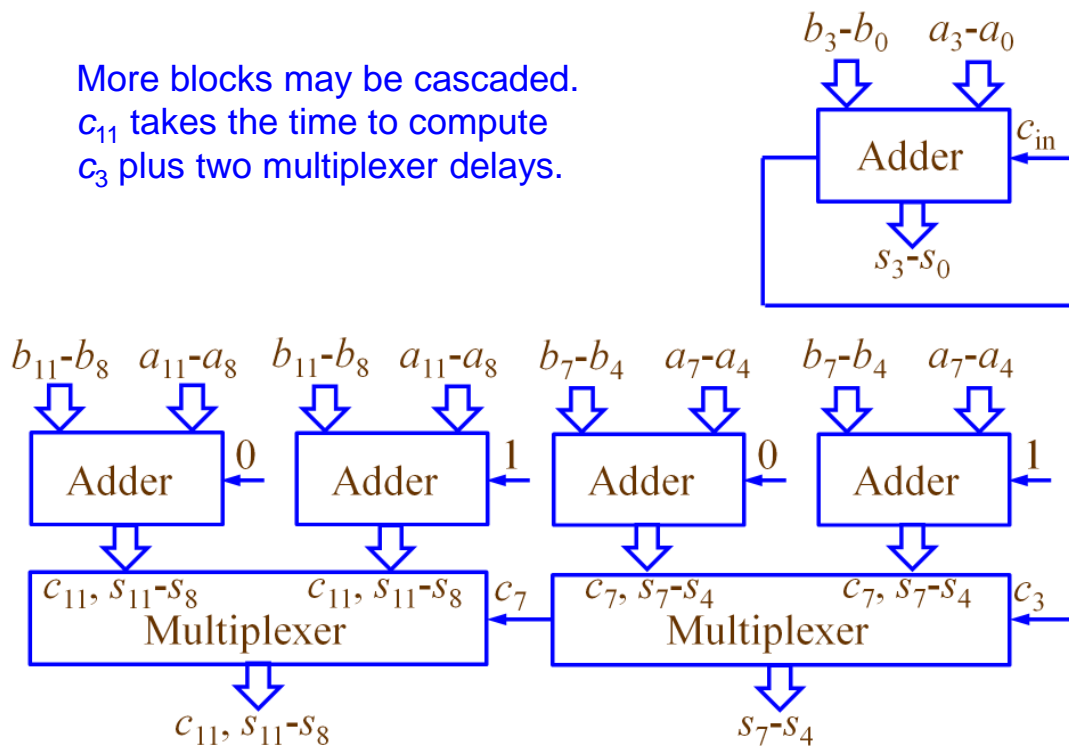
More blocks may be cascaded.  
 $c_{11}$  takes the time to compute  $c_3$  plus two multiplexer delays.



20

The time to compute  $c_3$  may itself be reduced.

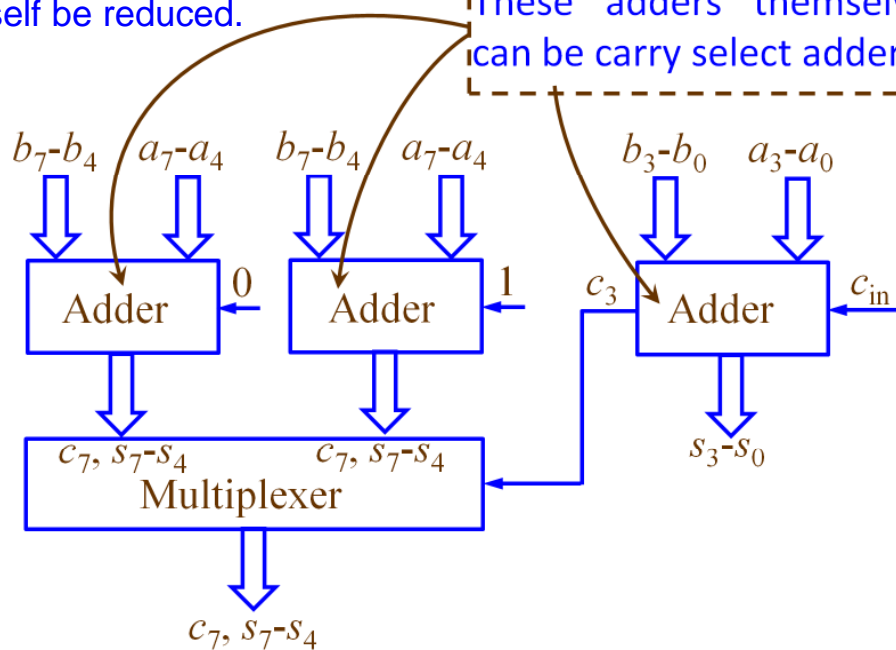These adders themselves can be carry select adders.



21


## Carry Save Adder

Consider the addition of 2 numbers  $A$  and  $B$  where

$$A = [a_{N-1}, \dots, a_n, \dots, a_1, a_0]$$


$$B = [b_{N-1}, \dots, b_n, \dots, b_1, b_0]$$

 Suppose that the addition of  $a_0, b_0$  and  $c_{in}$  produces sum  $s_0$  and carry  $c_0$ . In general, the addition of  $a_n, b_n$  and  $c_{n-1}$  produces sum  $s_n$  and carry  $c_n$ .  $c_n$  is added to  $a_{n+1}$  and  $b_{n+1}$  to produce  $c_{n+1}$ . In a ripple carry adder, the carry-bit ripples "horizontally".



22

 
Now consider the addition of 3 numbers  $A$ ,  $B$ , and  $D$  where  $D = [d_{N-1}, \dots, d_n, \dots, d_1, d_0]$ . The addition can be done in the following way.



In the above scheme,  $c_n$  is not added to  $a_{n+1}$  and  $b_{n+1}$  but is added in the full adder that adds  $d_{n+1}$ . The scheme avoided “horizontal” addition of carry-bit in the addition of  $A$  and  $B$ . Nevertheless, the carry bits at the output of the full adders must still be added “horizontally”.

23

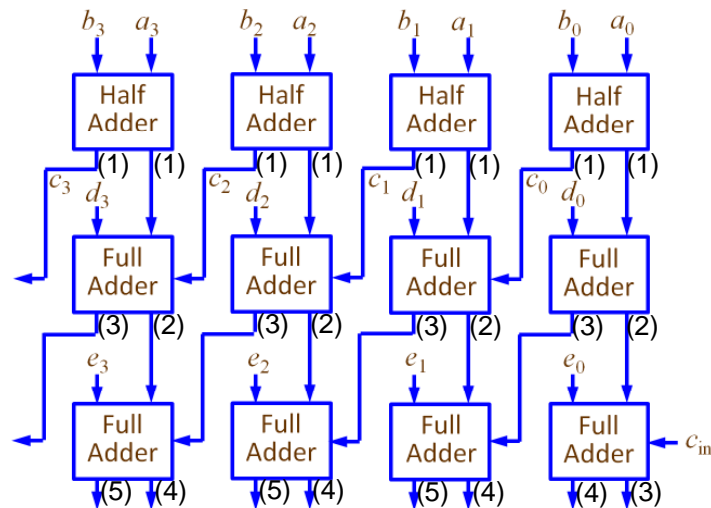
Now consider the addition of 4 numbers  $A$ ,  $B$ ,  $D$ , and  $E$  where  $E = [e_{N-1}, \dots, e_n, \dots, e_1, e_0]$ .



The carry bits for the last row of full adders must still be added “horizontally”.

24


Now consider the addition of 5 numbers.

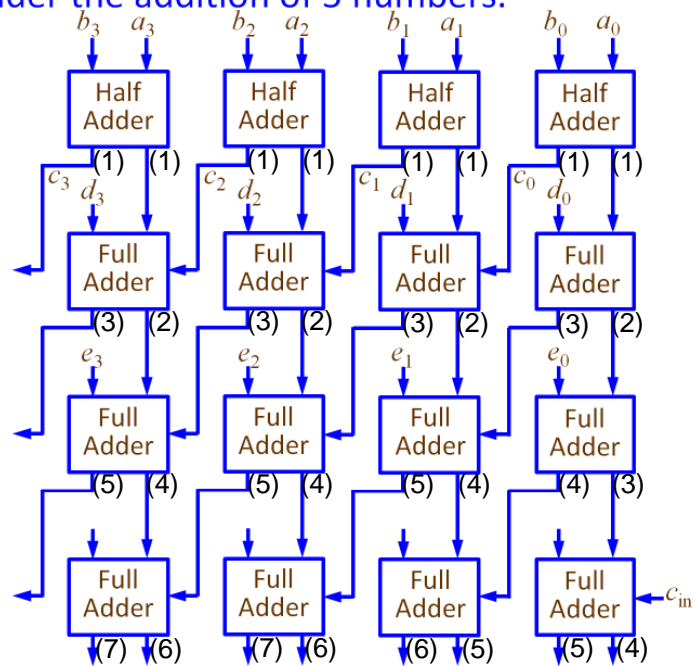

Only the carry bits for the last row ripple “horizontally”.

25

## Pipelined Adder

 


Suppose that the time required by an adder is  $x$  seconds.

The time required to compute the sum will be  $2x$  seconds.

26

## A pipelined full adder

 


$X$	$Y$	$Z$	$C$	$S$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

27

Cascading 2 full adders:


$$\begin{array}{r}
 A_1 \ A_0 \\
 + \ B_1 \ B_0 \\
 \hline
 S_2 \ S_1 \ S_0
 \end{array}$$

L = latch

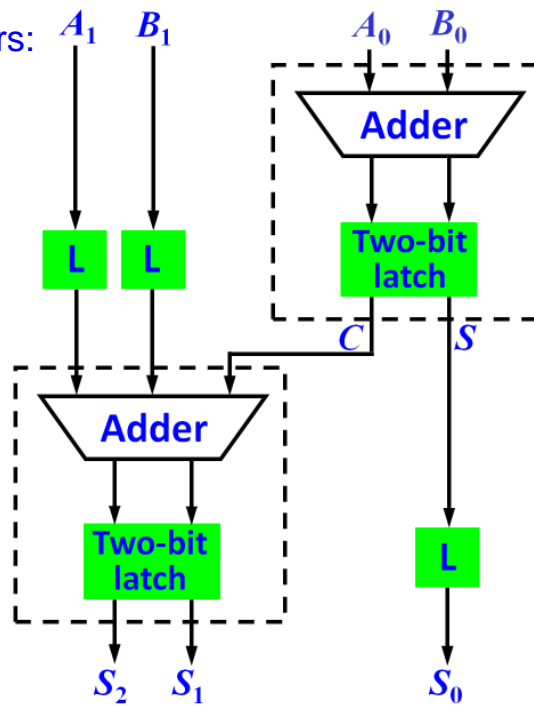

28

Cascading  $N$  full adders:

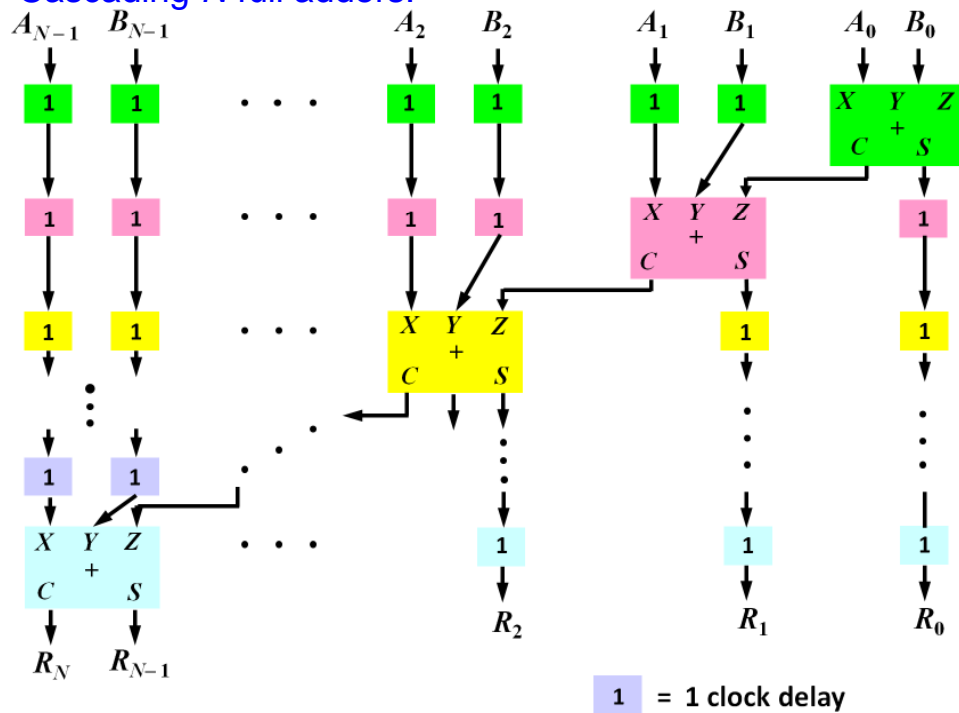

29

## Floating-Point Adder

Operands:  $A$ ,  $B$

Step 1: Compare  $A$  and  $B$

Step 2: Data alignment


Step 3: Add

Step 4: Determine number of leading zeros

Step 5: Normalization

$$\begin{aligned}
 &0.9878 \times 10^5 + 0.8934 \times 10^4 \\
 &= 0.9878 \times 10^5 + 0.08934 \times 10^5 \\
 &= 1.07714 \times 10^5 \\
 &= 0.107714 \times 10^6
 \end{aligned}$$

30

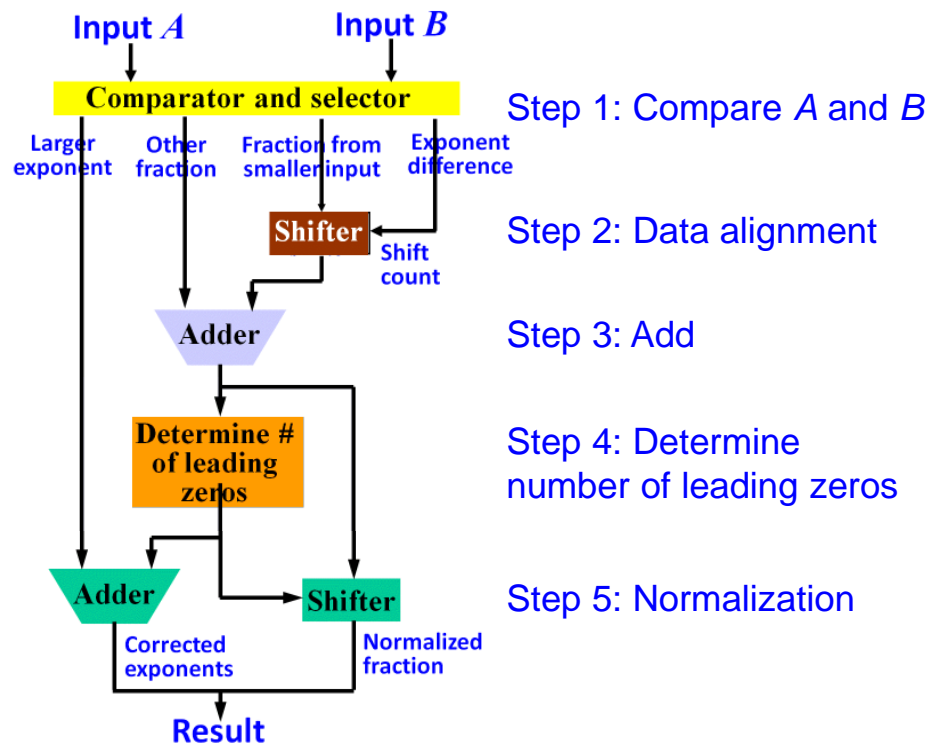

31

## Multiplier

37



## Integer-Power-of-Two Multiplier

$$(101000)_{2's} = -24$$

$$(110100)_{2's} = -12$$

$$(111010)_{2's} = -6$$

$$(111101)_{2's} = -3$$

$$(010100)_{2's} = 20$$

$$(001010)_{2's} = 10$$

$$(000101)_{2's} = 5$$



Shifting a two's complement number to the right (with sign extension) by 1 place has the effect of dividing the number by two.

Shifting a two's complement number to the right (with sign extension) by  $K$  places has the effect of dividing the number by  $2^K$ .

Thus, multiplying a number by an integer-power-of-two is a very simple process.


38

Multiplying by  $2^{-K}$

  


39

 Variable shifter: shift by  $K$  bits where  $0 \leq K \leq 7$



40

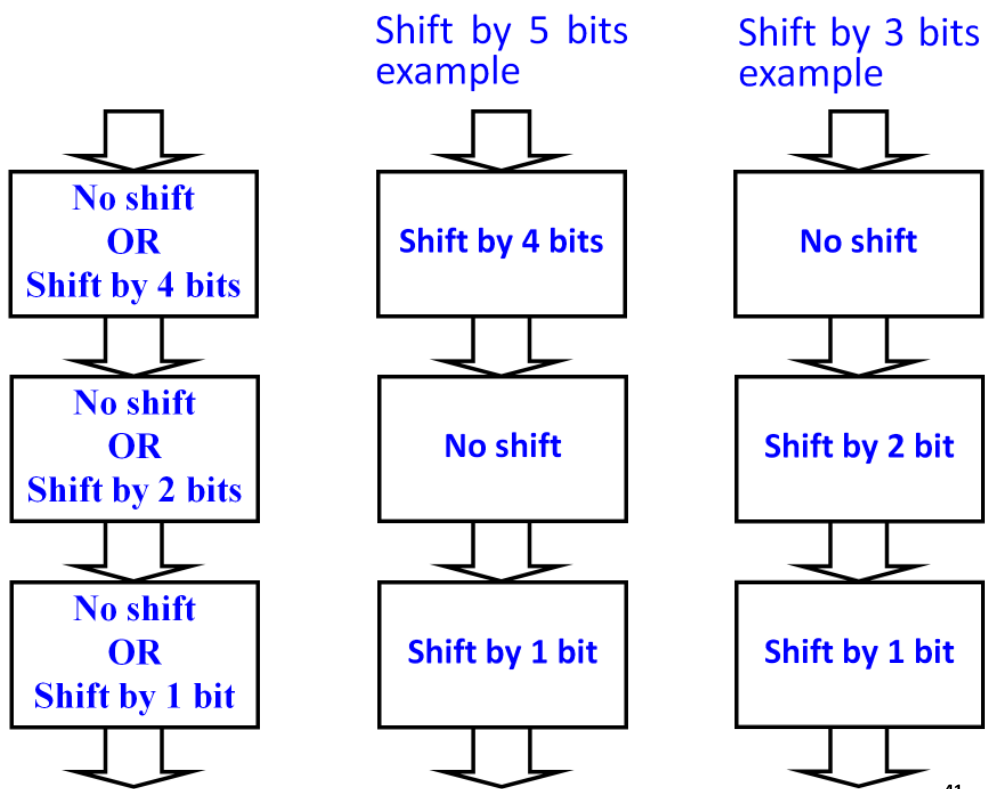

41

# Booth Multiplier

Multiply  $(6375)_{10} \times (99)_{10}$

$$\begin{aligned}(6375)_{10} \times (99)_{10} &= (6375)_{10} \times (100 - 1)_{10} \\ &= (637500)_{10} - (6375)_{10} \\ &= (631125)_{10}\end{aligned}$$

Multiply  $A \times (00011110)_{2's} = A \times (001000-10)_{2's}$

$$= A \times (00100000)_{2's} - A \times (00000010)_{2's}$$

42

Algorithm:

2  $n$ -bit numbers  $A, B$

Example:

$n = 4$

$A = (0011)_{2's} = 3$


$B = (1100)_{2's} = -4$

Precompute:

$A_+ = A, n+1$  zeros

$A_- = -A, n+1$  zeros

$P = n$  zeros,  $B, 1$  zero

 

43

Loop  $n$  times:

If 2 LSB's of  $P = 01$ ,  $P \leftarrow P + A_+$

$$A \times (00011110)_{2's} = A \times (001000-10)_{2's}$$

$\Rightarrow$  Add  $2^5 A$  to the product

If 2 LSB's of  $P = 10$ ,  $P \leftarrow P + A_-$

$$A \times (00011110)_{2's} = A \times (001000-10)_{2's}$$

$\Rightarrow$  Subtract  $2^1 A$  from the product

If 2 LSB's of  $P = 00$  or  $11$ , do nothing

$$A \times (00011110)_{2's} = A \times (001000-10)_{2's}$$

$\Rightarrow$  Do nothing


Shift  $P$  right by 1 bit

Brings next bit of  $B$   
Effectively shifts  $A_+$ ,  $A_-$  to the left, or  
multiplies  $2^i A$  by 2

Final product =  $P$  without the implicit bit


44

 Example:  $A = 0011 = 3$ ,  $B = 1100 = -4$




45

 Example:  $A = 0011 = 3$ ,  $B = 1100 = -4$




46

 Example:  $A = 0011 = 3$ ,  $B = 1100 = -4$



47

 Example:  $A = 0011 = 3$ ,  $B = 1100 = -4$




Final product  $P = 1111\ 0100 = -12$

48
 
## Wallace Tree Multiplier

2's complement multiplication: multiply 7 and 3




Adding partial product bits = counting number of 1's

Wallace tree uses layers of half/full adders to add these bits until only 2 bits are left in each position.

Adding these two numbers give the result.

49

 Multiply  $a_3a_2a_1a_0$  with  $b_3b_2b_1b_0$  :



50

Multiplication of two  $n$ -bit numbers gives  $m_i$  partial product bits in the  $i$ -th position, where  $m_i \leq n$ .

In a reduction layer,  $m_i$  partial product bits are reduced to  $\lceil \frac{m_i}{3} \rceil$  bits.

Since the  $(i-1)$ th position generates  $\text{round}(\frac{m_{i-1}}{3})$  carries, number of bits in the  $i$ -th position is reduced to:

$$\lceil \frac{m_i}{3} \rceil + \text{round}(\frac{m_{i-1}}{3})$$

$n=4$  example: Initial  $m_i = 1, 2, 3, 4, 3, 2, 1$  for  $i = 0$  to 6.

After reduction layer 1,  $m_4 = 3$  reduces to:

$$\lceil \frac{m_4}{3} \rceil + \text{round}(\frac{m_3}{3}) = \lceil \frac{3}{3} \rceil + \text{round}(\frac{4}{3}) = 1 + 1 = 2$$

Wallace tree multiplier is faster since it takes  $\log(n)$  time.

51